

- 15.10.** A  $70\text{-}\Omega$  high-frequency lossless line is used at a frequency where  $\lambda = 80\text{ cm}$  with a load at  $x = 0$  of  $(140 + j91)\text{ }\Omega$ . Use the Smith Chart to find:  $\Gamma_R$ , VSWR, distance to the first voltage maximum from the load, distance to the first voltage minimum from the load, the impedance at  $V_{\max}$ , the impedance at  $V_{\min}$ , the input impedance for a section of line that is  $54\text{ cm}$  long, and the input admittance.



On the Smith Chart plot the normalized load  $Z_R/R_0 = 2 + j1.3$ , as shown in Fig. 15-21. Draw a radial line from the center through this point to the outer  $\lambda$ -circle. Read the angle of  $\Gamma_R$  on the angle scale:  $\phi_R = 29^\circ$ . Measure the distance from the center to the  $z$ -point and determine the magnitudes of  $\Gamma_R$  and VSWR from the scales at the bottom of the chart.

$$|\Gamma_R| = 0.50 \quad \text{VSWR} = 3.0 \quad \text{and} \quad \Gamma_R = 0.5 \angle 29^\circ$$

Draw a circle at the center passing through the plotted normalized impedance. Note that this circle intersects the horizontal line at  $3 + j0$ . This point of intersection could be used to determine the VSWR instead of the bottom scale, because the circle represents a constant VSWR. Locate the intersection of the VSWR circle and the radial line from the center to the open-circuit point at the right of the  $z$ -chart. This intersection is the point where the voltage is a maximum (the current is a

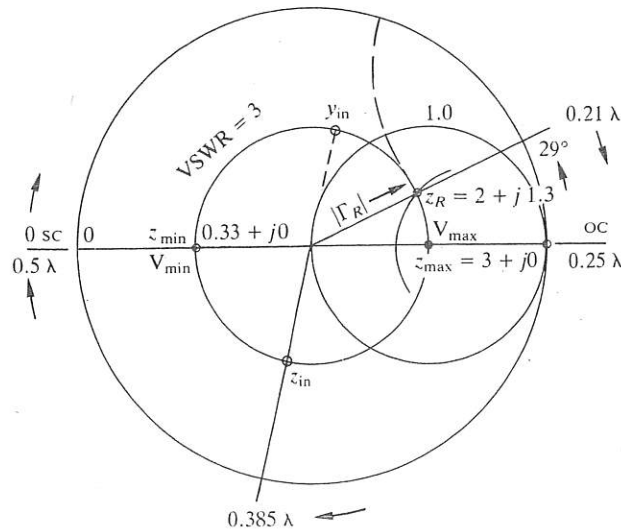


Fig. 15-21

minimum) and the impedance is a maximum. The normalized impedance at this point is  $3 + j0$ , whence  $Z_{\max} = 210 + j0\text{ }\Omega$ . To find the distance from the load to the first  $V_{\max}$  use the outer scale (wavelengths toward the generator). The reference position is at  $0.21\lambda$  and the max. line is at  $0.25\lambda$ ; so the distance is  $0.04\lambda$  toward the generator, or  $3.2\text{ cm}$  from the load.

From the  $V_{\max}$  point move  $0.25\lambda$  toward the generator and locate the  $V_{\min}$  point. The normalized impedance is  $0.33 + j0$ , and  $Z_{\min} = 23.1 + j0\text{ }\Omega$ . The distance from the load to the first minimum is

$$0.25\lambda + 0.04\lambda = 0.29\lambda = 23.2\text{ cm}$$

To find the input impedance, move  $\frac{54}{80} = 0.675$  wavelengths from the load toward the generator, and read the normalized impedance. Once around the circle is  $0.5\lambda$ , so locate the point that is  $0.175\lambda$  from the load on the outer scale. The point is at  $0.21\lambda + 0.175\lambda = 0.385\lambda$ . Through this point draw a radial line and locate the intersection with the VSWR circle. The normal impedance is  $0.56 - j0.71$  and  $Z_{\text{in}} = 39.2 - j49.7\text{ }\Omega$ .

The normalized input admittance is located a diameter across on the chart, which corresponds to the inversion of a complex number. For  $z = 0.56 - j0.71$ ,  $y = 0.68 + j0.87$ ; therefore,

$$Y_{\text{in}} = \frac{y}{R_0} = (9.71 + j12.4)\text{ mS}$$